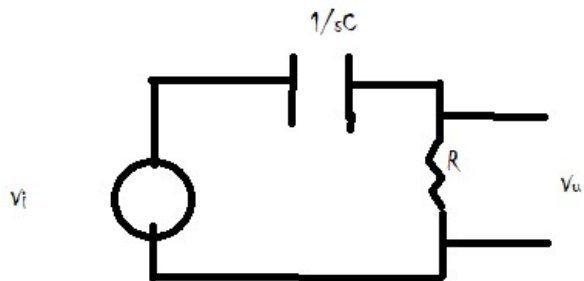


Circuito RC

Uscita sul resistore



$$V_i(s) = i(s) \left(R + \frac{1}{sC} \right) = \frac{V_R(s)}{R} \left(R + \frac{1}{sC} \right) \quad G(s) = \frac{V_R}{V_i} = \frac{sRC}{(sRC+1)}$$

$$G(s) = \frac{3}{s + 45} \quad g(t) = 3e^{-45t}$$

$$G(s) = \frac{RCs}{1 + RCs}$$

$$V(s) = \frac{K}{s}$$

$$V_r(s) = \frac{K}{s} \frac{RCs}{1+RCs} = \frac{RC}{1+RCs} = \frac{RC}{RC\left(\frac{1}{RC}+s\right)} = \frac{K}{\left(\frac{1}{RC}+s\right)}$$

$$V_R(t) = Ke^{-\frac{t}{RC}}$$



$$R=10000\Omega$$

$$C=10\text{nF}=10^{-8}\text{F}$$

Caso particolare $\omega=30\text{ Hz}$

$$R*C=10^{-4}\text{s}$$

$$|G(\omega)|=\omega R*C/(1+(\omega RC)^2)^{1/2}$$

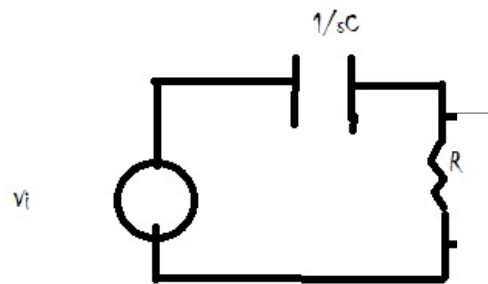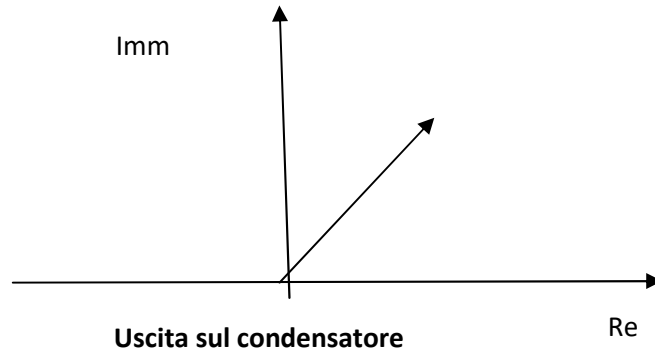

$$V_i(s) = V_R(s) + V_c(s) = R * i(s) + \frac{1}{sC} i(s) = i(s) \left(R + \frac{1}{sC} \right) = V_c(s) * sC \left(R + \frac{1}{sC} \right) = V_c sC \left(\frac{sRC + 1}{sC} \right) = V_c(1 + sRC)$$

$$\frac{V_i(s)}{v_c(s)} = 1 + sRC \quad \frac{V_c(s)}{V_i(s)} = \frac{1}{1 + sRC} = \frac{1}{RC \left(\frac{1}{RC} + s \right)}$$

$$V_i(s) = \frac{k}{s} \quad V_c(s) = \frac{k}{s} \frac{1}{RC \left(\frac{1}{RC} + s \right)} = \frac{A}{s} + \frac{B}{\frac{1}{RC} + s}$$

$$V_u(t) = A + B e^{-\frac{t}{RC}}$$

Caso generale: diagrammi di Bode

Si valuta l'andamento di un sistema o di un circuito per tutte le frequenze possibili (0; +∞)

Funzione di trasferimento di un circuito RC con uscita sul resistore

zero $s=0$; polo $s=-1/RC=-10000$

$$G(s) = \frac{10^{-4}s}{1+s10^{-4}}$$

$$|G(s)| = -80 + 20 \log |s| - 20 \log |1+s10^{-4}|$$

$$\phi(s) = 90^\circ - \arctg(s \cdot 10^{-4}) =$$

1. $s=1000$ $\phi(1000) = -\arctg(0.1) = 0$
2. $s=10000$ $\phi(10000) = -\arctg(1) = -45^\circ$
3. $s=100000$ $\phi(100000) = -\arctg(10) = -90$

Grafico parziale


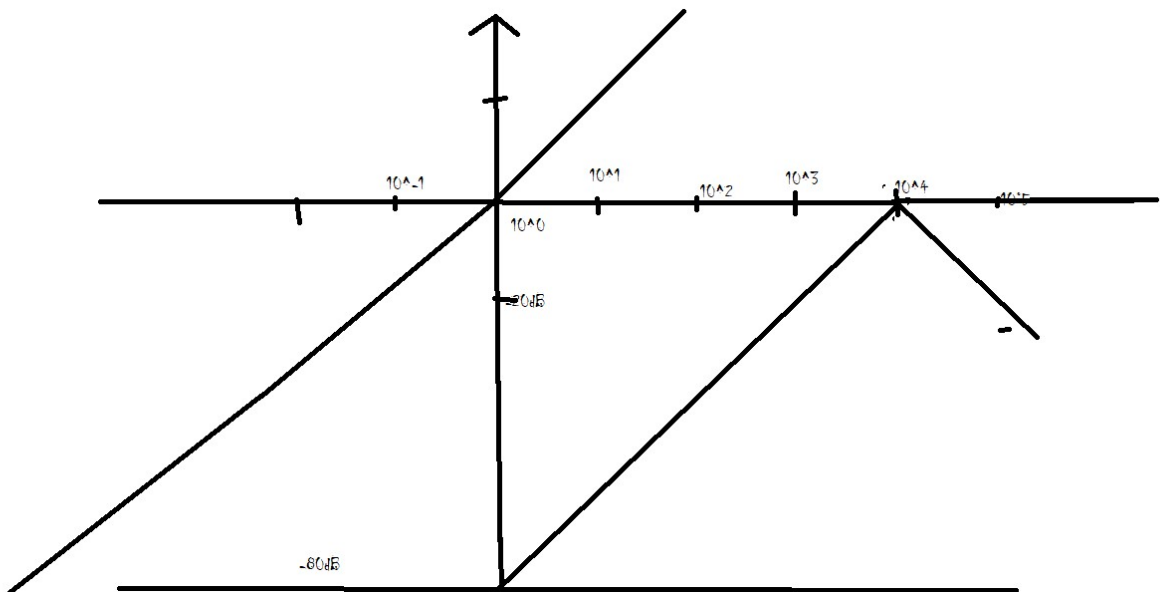


Grafico totale

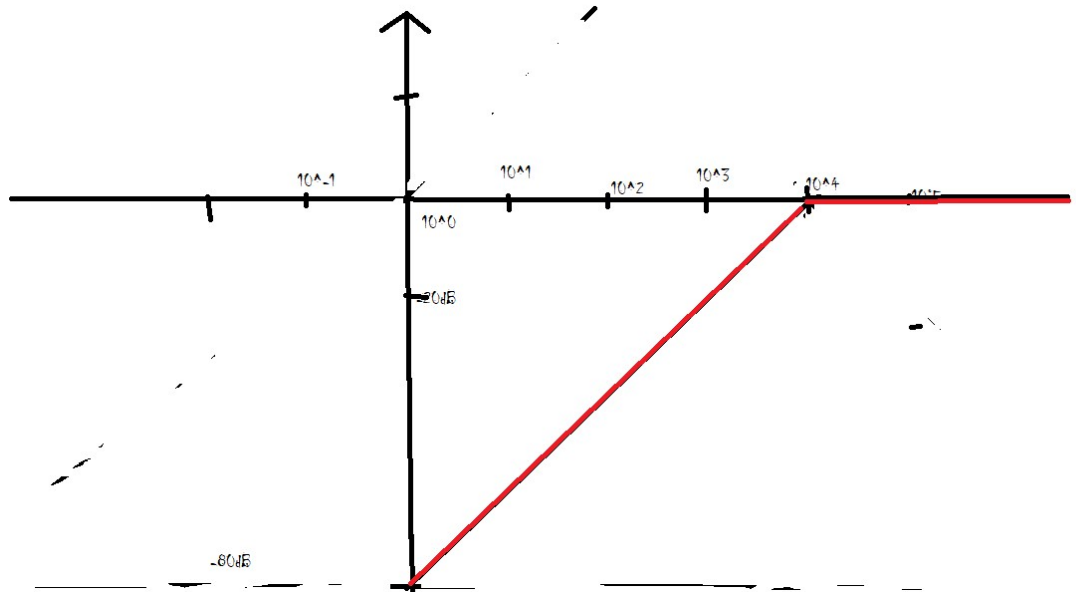

Sfasamento

